

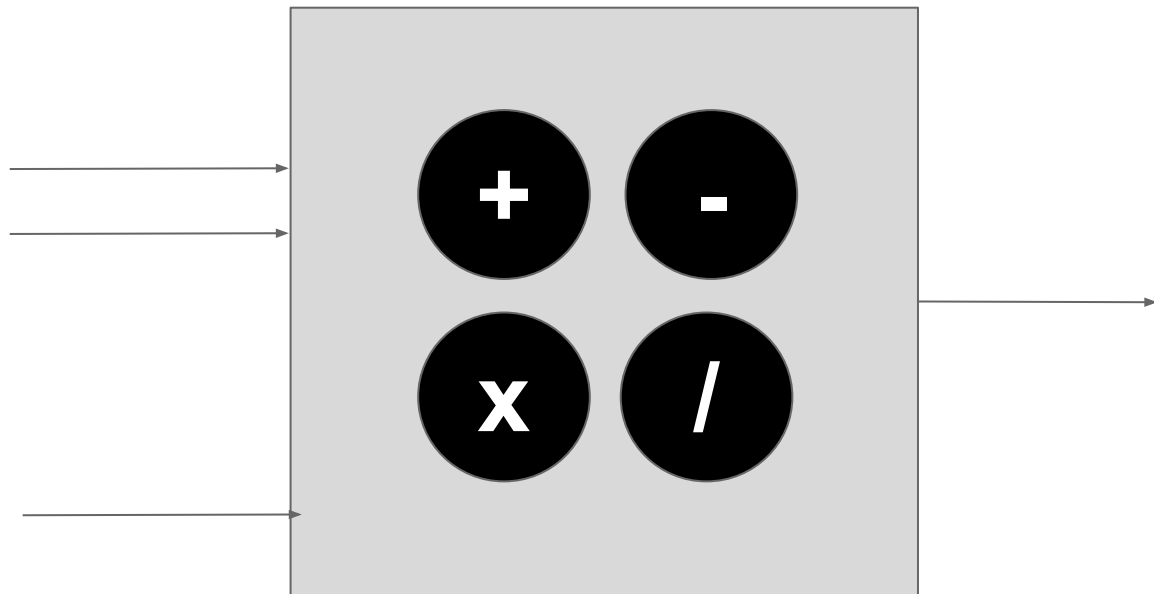


# Conditional functions


# Functions so far...

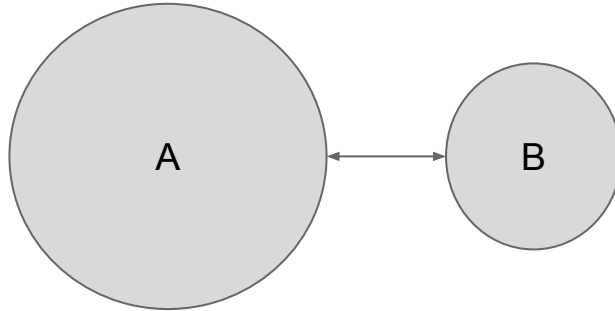

# Difference between two numbers

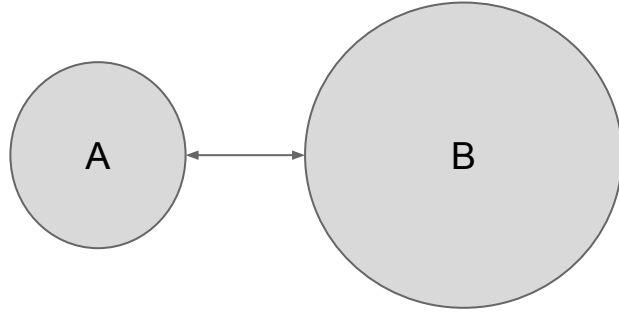

**So difference:**

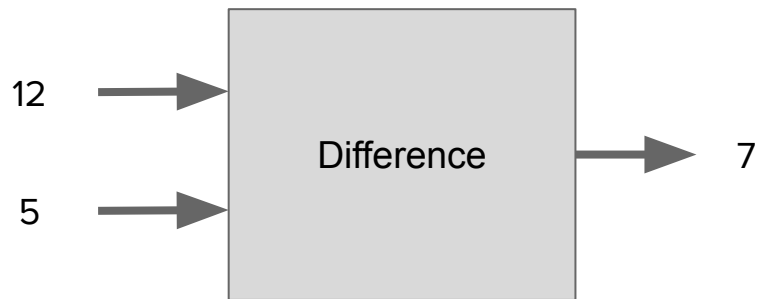


# How do we solve this:

You will say it's very easy:


**if firstInput > secondInput then output (firstInput - secondInput)**

**Otherwise output (secondInput - firstInput)**

**You made an assumption:**

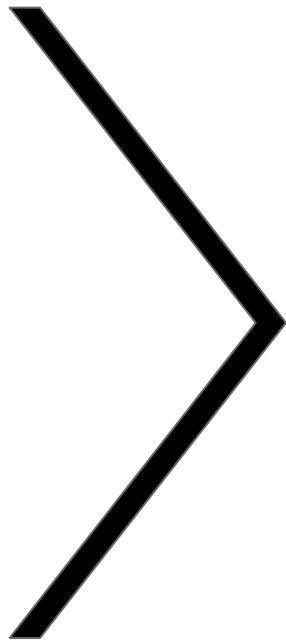


**Can you do this comparison?**

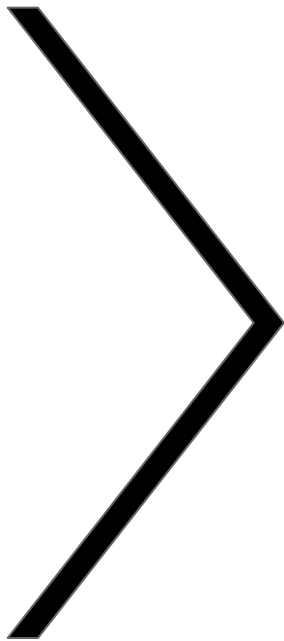

## How about now?

Position  
(100, 20) on  
the screen

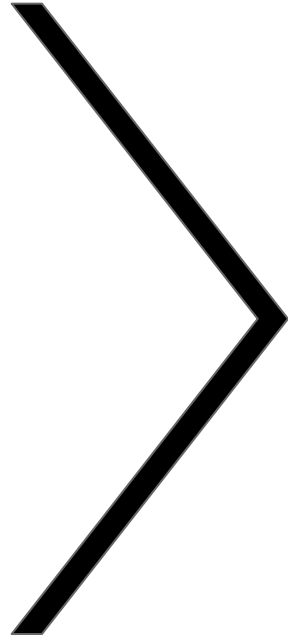

Position  
(20, 40) on  
the screen



**So what makes something GREATER  
than something else**

**Numbers - Integers and Real - are obviously comparable.**

$2 > 1 \implies \text{YES}$


$11000 > 122 \implies \text{DEFINITELY}$

$3.141592653589 > 3.1 \implies \text{YEAH!!}$

**But how is the computer comparing them?**

$$\begin{array}{r} 123 > 50 \\ \hline 1 > 0 \end{array}$$

# Review : Gates

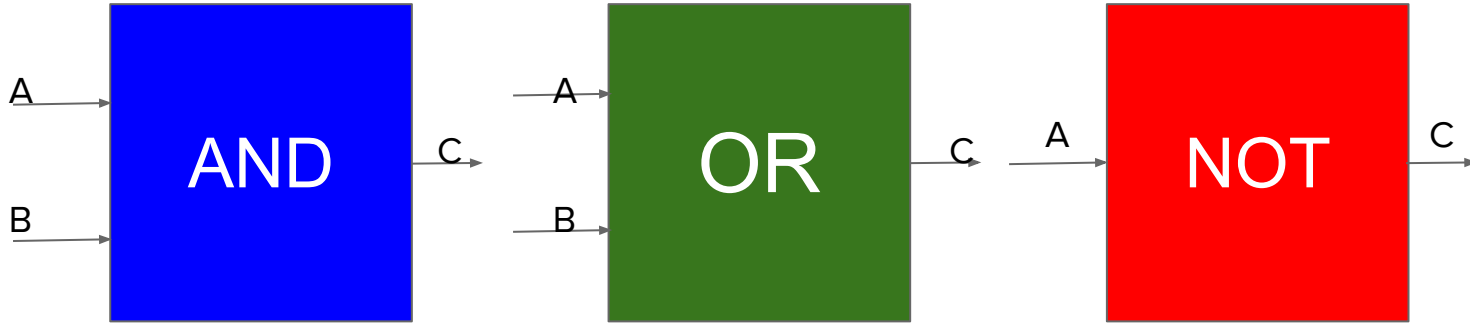

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1


A	C
0	1
1	0

# Comparing 1s and 0s



A	B	$A > B$
0	0	0
0	1	0
1	0	1
1	1	0

# Comparing 1s and 0s

A	B	$A > B$
0	0	0
0	1	0
1	0	1
1	1	0

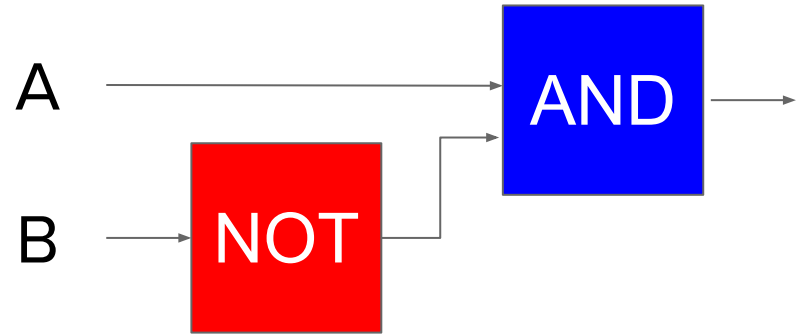

# Comparing the other way around:

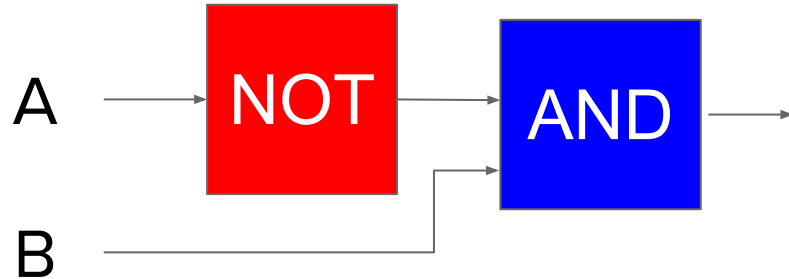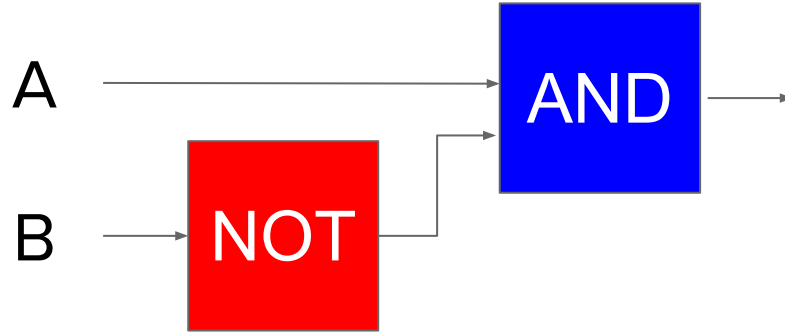

# Representing numbers

$$123 = 3 \times 1 + 2 \times 10 + 1 \times 100$$



# Representing numbers



$$123 = 1 \times 2^0 + 1 \times 2^1 + 0 \times 2^2 + 1 \times 2^3 + 1 \times 2^4 + \\ 1 \times 2^5 + 1 \times 2^6$$




Reverse order

# LOGIC GATES

① Consider a simple circuit:-

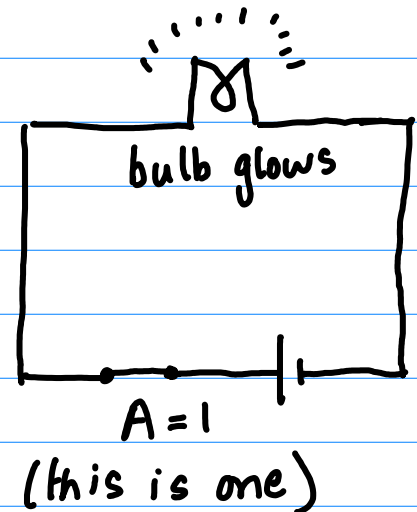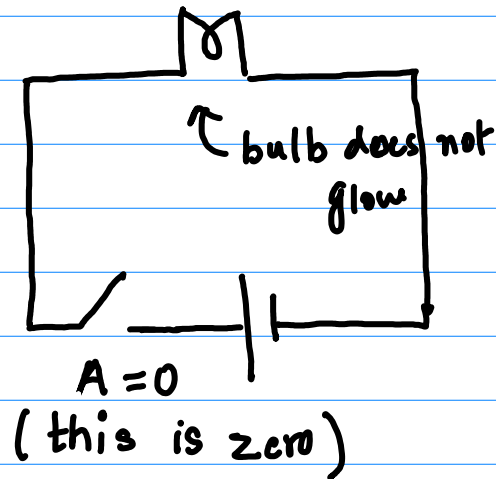

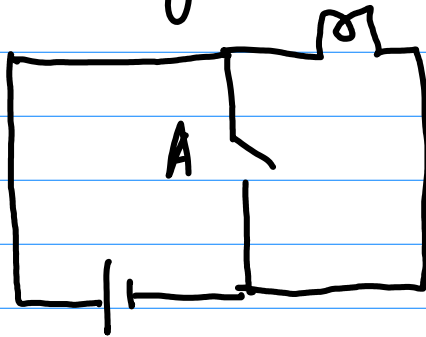② We can arrange the switch A differently




**NOT**

In this arrangement,  
when  $A=0$ , the bulb glows  
when  $A=1$  the bulb does not glow.

The bulb is then  $NOT(A)$

A	Bulb = not A
0	1
1	0

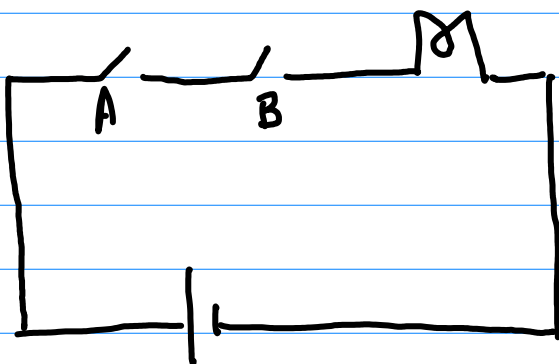③ Let us consider next a circuit with two switches




AND

Only if both A and B are 1 the bulb will glow...

A	B	Bulb = A and B
0	0	0
0	1	0
1	0	0
1	1	1

④ Finally let's consider this one →

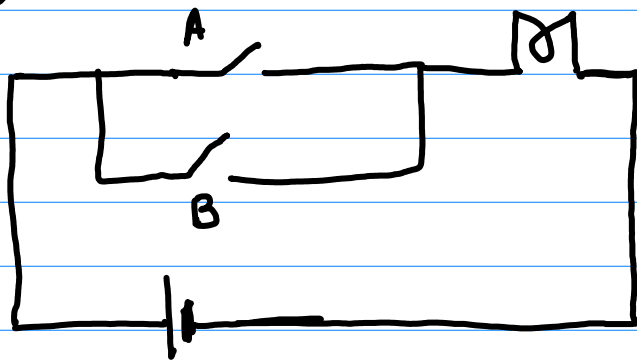

OR

A	B	Bulb = A or B
0	0	0
0	1	1
1	0	1
1	1	1

If either switch A or B is 1, the bulb glows.

⑤ Using AND, OR, NOT to do comparisons

A	B	$A > B$	$A < B$	$A == B$
0	0	0	0	1
0	1	0	1	0
1	0	1	0	0
1	1	0	0	1

